

WHICH SWITCH IS WHAT SWITCH?


A USEFUL GUIDE FROM **socketstore**

Let us delve into the world of switches and circuits to explain what they are and where they're to be used...

HEY SOCKETSTORE... WHAT IS A NORMAL SWITCH?

there are 2 types of normal switches...


THE ONE WAY SWITCH

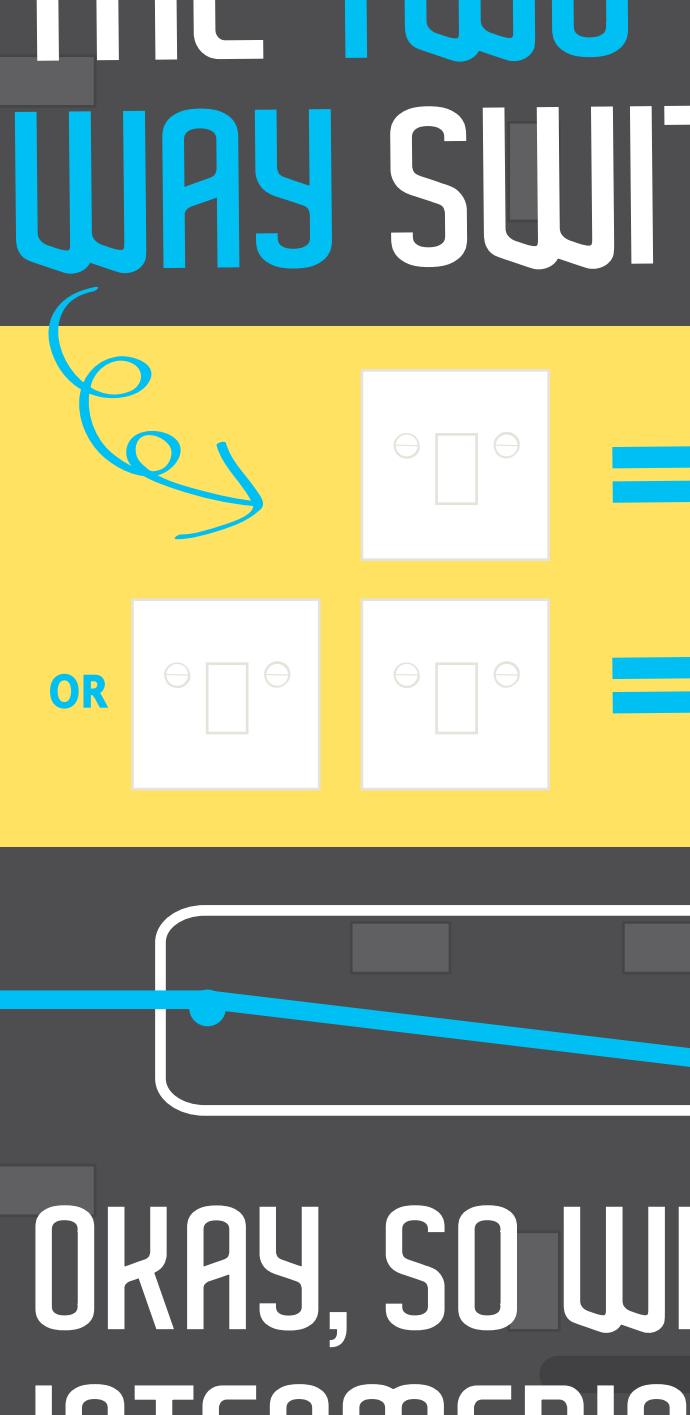


the technical bit



THE TWO WAY SWITCH

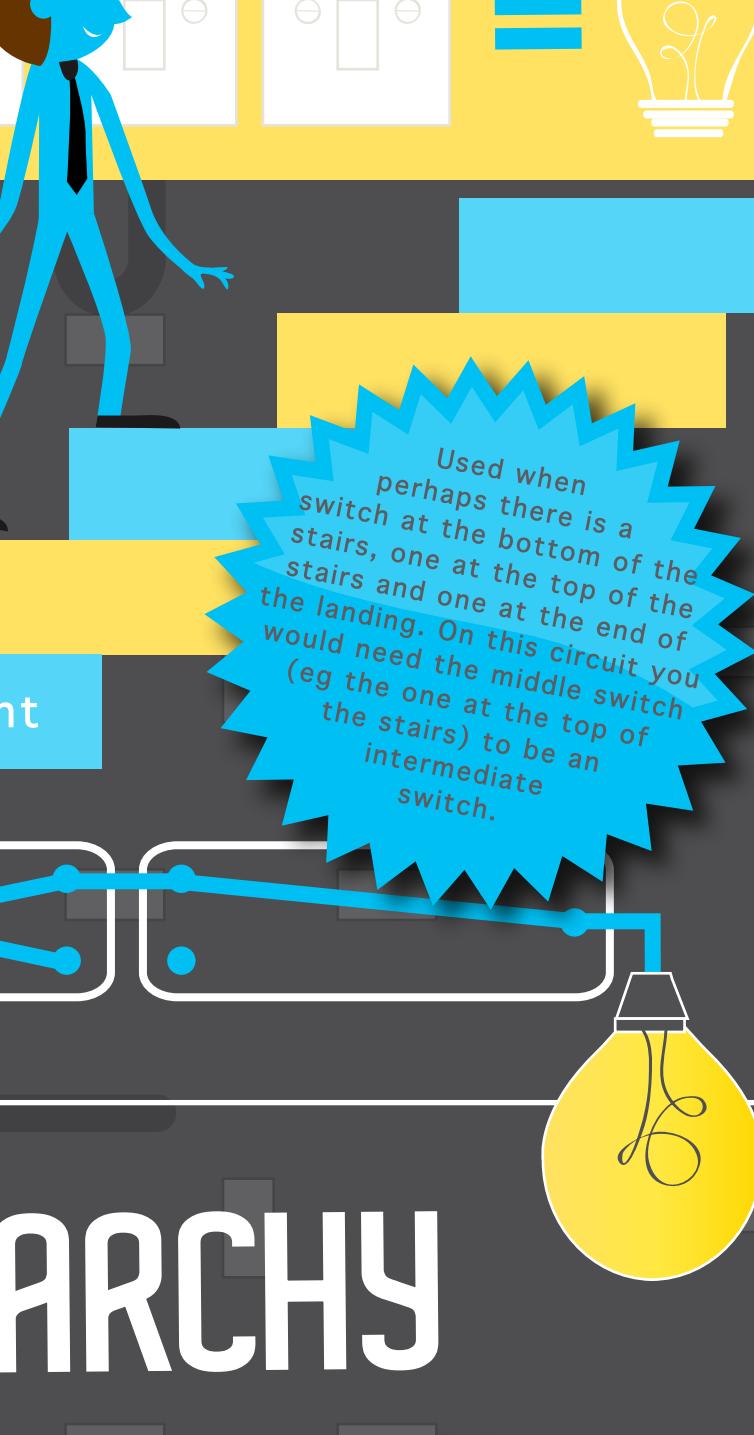

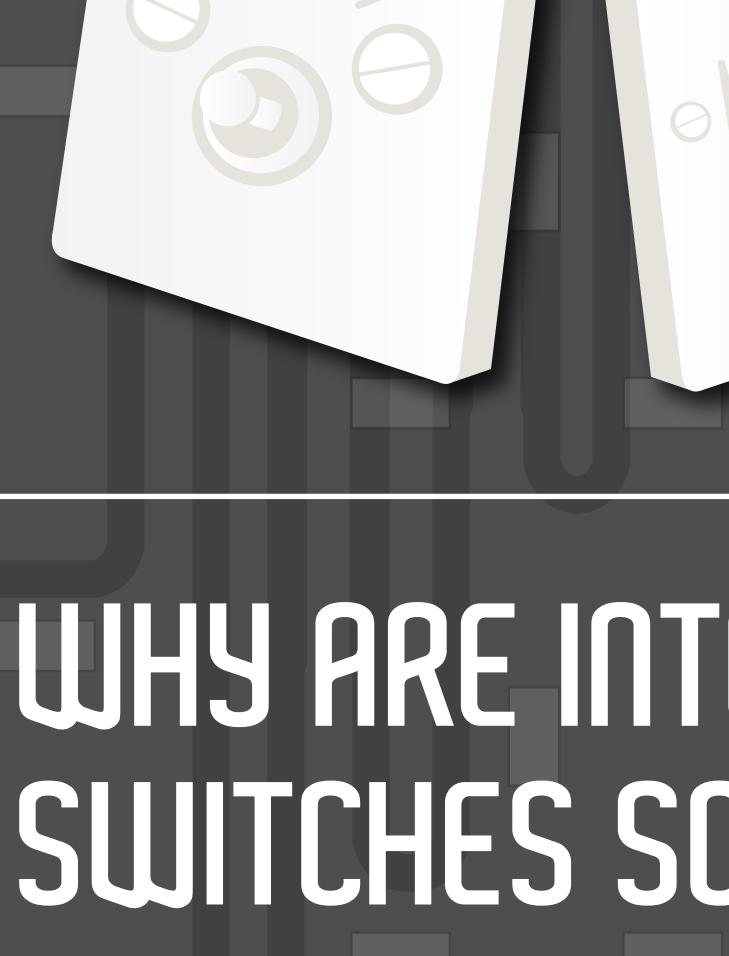INTERMEDIATE SWITCH = BIG BOY OF LIGHT SWITCHES



3 switches to one light


Used when perhaps there is a switch at the bottom of the stairs, one at the top of the landing. On this circuit you would need the middle switch (eg the one at the top of the stairs) to be an intermediate switch.

SWITCH HIERARCHY

1ST
INTERMEDIATE

2ND
TWO WAY

3RD
ONE WAY

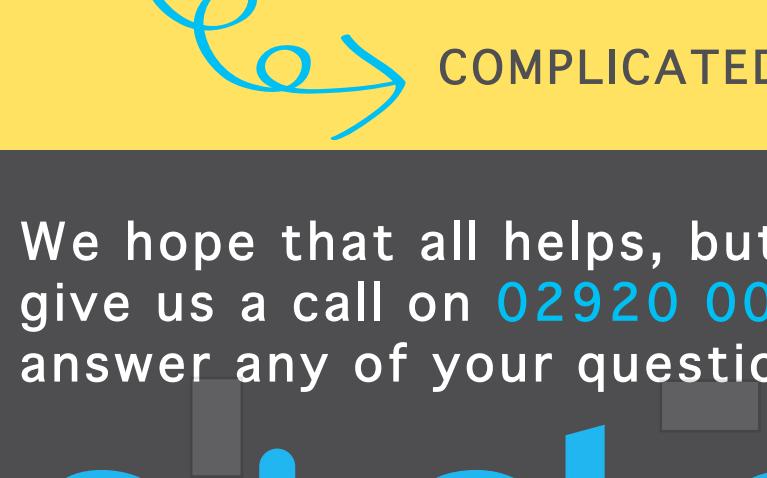

SIMPLE ONE WAY CIRCUIT

because the circuits are so much more complex they cost a lot more to manufacture



COMPLICATED INTERMEDIATE CIRCUIT

We hope that all helps, but of course if you are still unsure give us a call on 02920 004887 and we'd be happy to answer any of your questions.

socketstore

Infographic design by www.jessicadraws.com